

# Experiment 6: Musical Tune Player

Prasann Viswanathan, Roll Number 190070047  
EE-214, WEL, IIT Bombay  
April 3rd, 2021

## Overview of the experiment:

The purpose of this experiment was to use FSM theory to play a sequence of musical notes in order to create a melodious tune. This was to be done using krypton board and the basic speaker set up of a previous lab.

For this experiment, we needed three VHDL files – toneGenerator from lab 5, music.vhd and song\_tb, provided to us by the TAs. Modifications needed to be made only in music.vhd. We had to complete the code in order to properly map indices under each note to the correct subsequent note. Also we had to go in steps of 0.25s (4Hz) requiring some more careful mappings to play the given musical piece.

## Approach to the experiment:

The musical piece to be played was given as:

Note	Sa	Ga	Sa	Ga	Sa	Ga	Ma	Ga	Re	Sa
Duration	0.5s	0.5s	0.5s	0.5s	0.5s	0.5s	0.25s	0.25s	0.25s	0.25s
Count	1, 2	3, 4					13			16
Note	Ni	Re	Ni	Re	Ni	Re	Ga	Re	Sa	Ni
Duration	0.5s	0.5s	0.5s	0.5s	0.5s	0.5s	0.25s	0.25s	0.25s	0.25s
Count										32

Table 1: Notes Table

As a result, we were to map the correct indices under each block to the correct following note. Here is the mapping –

Sa(1, 5, 9) → Sa, Sa(2, 6, 10) → Ga, Sa(16, 31) → Ni  
Re(15, 30) → Sa, Re(19, 23, 27) → Re, Re(20, 24) → Ni, Re(28) → Ga  
Ga(3, 7, 11) → Ga, Ga(4, 8) → Sa, Ga(12) → Ma, Ga(14, 29) → Re  
Ma(13) → Ga  
Ni(17, 21, 25) → Ni, Ni(18, 22, 26) → Re, Ni(32) → Sa

## Design document and VHDL code if relevant:

As mentioned in overview, we used three VHDL files to implement this musical tune player:

**toneGenerator** : From lab 5, maps switches to different frequencies played by speaker.

Switch 1 → Sa, ..., Switch 7 → Ni

**song\_tb** : Provided by the TAs. No modification was necessary. Used in order to test the RTL simulation of our device.

**music** : The main logic for this lab. We had to implement the FSM part of the design in this file. Mainly the architecture which is shown here:-

architecture fsm of music is

type state\_type is (Silent,sa,ga,ma,re,ni);

signal y\_present : state\_type;

signal LED\_2:std\_logic\_vector(7 downto 0);

signal count : integer := 0 ;

signal clock\_music:std\_logic :='0';

component toneGenerator is

port (toneOut : out std\_logic; --this pin will give your notes output

clk : in std\_logic;

LED : out std\_logic\_vector(7 downto 0);

switch : in std\_logic\_vector(7 downto 0));

end component;

begin

process(clk\_50,resetn,y\_present,clock\_music) -- Fill sensitivity list

variable y\_next\_var : state\_type;

variable n\_count : integer := 0;

variable timecounter : integer range 0 to 1E8 := 0;

begin

y\_next\_var := y\_present;

n\_count := count;

case y\_present is

when Silent=>

y\_next\_var := sa;

LED\_2 <= (0 =>'0',others =>'0');

WHEN sa => --if the machine in Sa state

if((n\_count=2) or (n\_count=6) or (n\_count=10)) then

y\_next\_var := ga;

elsif ((n\_count=16) or (n\_count=31)) then

y\_next\_var := ni;

else

y\_next\_var := sa;

end if;

LED\_2 <= (0=>'1',others=>'0');

WHEN re =>

if ((n\_count=15) or (n\_count=30)) then

y\_next\_var := sa;

elsif ((n\_count=20) or (n\_count=24)) then

y\_next\_var := ni;

elsif((n\_count = 28)) then

y\_next\_var := ga;

else

y\_next\_var := re;

end if;

```

        LED_2 <= (1=>'1',others=>'0');

    WHEN ga =>
        if ((n_count=4) or (n_count=8)) then
            y_next_var := sa;
        elsif ((n_count=12)) then
            y_next_var := ma;
        elsif ((n_count=14) or (n_count=29)) then
            y_next_var := re;
        else
            y_next_var := ga;
        end if;
        LED_2 <= (2=>'1',others=>'0');

    WHEN ma =>
        y_next_var := ga;
        LED_2 <= (3=>'1',others=>'0');

    WHEN ni =>
        if((n_count=18) or (n_count=22) or (n_count=26)) then
            y_next_var := re;
        elsif ((n_count=32)) then
            y_next_var := sa;
        else
            y_next_var := ni;
        end if;
        LED_2 <= (6=>'1',others=>'0');
END CASE ;

--
generate 4Hz clock (0.25s time period) from 50MHz clock (clock_music)
if (clk_50 = '1' and clk_50' event) then
    if (resetn = '0') then
        if timecounter = 6250000 then -- The cycles in which clk is 1 or 0
            timecounter := 1;
            clock_music <= not clock_music;
        else
            timecounter := timecounter + 1;
        end if;
    elsif resetn = '1' then
        timecounter := 1;
        clock_music <= '0';
    end if;
end if;

--
state transition
if (clock_music = '1' and clock_music' event) then
    if (resetn = '1') then
        y_present <= Silent;
        count <= 0;
    else
        y_present <= y_next_var;
        count <= n_count + 1;
    end if;
end if;

```


end process;

TG: toneGenerator

port map(toneOut, clk\_50, LED, LED\_2);

end fsm;

## RTL View:

 

## State Transition Diagram:-



## DUT Input/Output Format:


NA

The screenshot displays the ModelSim - INTEL FPGA STARTER EDITION 2020.1 software interface. The top window shows a project tree with files like 'Design', 'Design', 'Design', and 'Design'. The main window displays a timing diagram with a green signal trace. The bottom window shows a command prompt with the following text: 'Loading ieee.std\_logic\_1164(body); Loading work.schematic; Loading work.main; Loading work.tonegenerator; add wave \*; view structure; .main\_package.interior.cb.body.struc; view signals; .main\_package.objects.interior.cb.body.tree; run -all'.

NA
----

# Pin Planning :

### Krypton Board Connections :

 

### Observations:

The speakers play the musical tune as desired. It keeps looping over itself unless a switch is pressed after which it stops.

Video link :

[https://drive.google.com/file/d/1jNUXD1\\_pkg8osc0CIsxDcnC26Gyk7ta3/view?usp=sharing](https://drive.google.com/file/d/1jNUXD1_pkg8osc0CIsxDcnC26Gyk7ta3/view?usp=sharing)

### References:

NA