

# Experiment 5: Musical Notes

Prasann Viswanathan, Roll Number 190070047  
EE-214, WEL, IIT Bombay  
March 27, 2021

## Overview of the experiment:

The purpose of the experiment was to play Musical notes' octet on a speaker using VHDL code. We use a sequential style VHDL code to generate frequencies corresponding to musical notes on the Krypton board which in turn is connected to a speaker. The inputs are given using the switches on the board and a clock of frequency 50MHz. The output source powering the speaker is PIN\_1 on Krypton board and LEDs to indicate which note is played. The frequencies for each note is created by making a simple counter using the clock divider technique. Each frequency has a different count which is calculated as  $50\text{MHz}/2f$ . We use a testbench which tests the code by simulating the output frequency for each of the switch inputs. The frequencies can be verified in the RTL simulation by checking the output's time periods. This verifies the functioning of the code on software. And, finally, the pin planning is done accordingly and svf is generated and parsed onto the Krypton board, the speaker is connected to the board through appropriate components and the hardware functioning is verified by checking the tone and LEDs for different switch inputs.

## Approach to the experiment:

The count to be given for different frequencies is calculated as  $50 \times 10^6 / (2 \times f)$ .

Note	Frequency	Count
Sa	240Hz	104168
Re	270Hz	92593
Ga	300Hz	83333
Ma	320Hz	78125
Pa	360Hz	69444
Dha	400Hz	62500
Ni	450Hz	56556
Sa(upper octave)	480Hz	52083

## Design document and VHDL code if relevant:

ToneGenerator\_tb: Acts as Testbench.  
ToneGenerator: Main logic, code template provided by TAs, some additions needed to be made.

### Architecture of ToneGenerator is:

```
architecture behavioral of toneGenerator is
begin
process(clk)
variable count_sa1 : integer := 0;
```

```

variable sa1 : std_logic := '0';
begin
if(clk = '1' and clk' event) then
    if(switch(0) = '1') then
        if (count_sa1 = 104167) then--240Hz
            count_sa1 := 1;
            sa1 := not sa1;
        else
            count_sa1 := count_sa1 + 1;
        end if;
        toneOut <= sa1;
        LED <= (0 => '1', others => '0');

    elsif(switch(1) = '1') then
        if (count_sa1 = 92593) then--270Hz
            count_sa1 := 1;
            sa1 := not sa1;
        else
            count_sa1 := count_sa1 + 1;
        end if;
        toneOut <= sa1;
        LED <= (1 => '1', others => '0');

    elsif(switch(2) = '1') then
        if (count_sa1 = 83333) then--300Hz
            count_sa1 := 1;
            sa1 := not sa1;
        else
            count_sa1 := count_sa1 + 1;
        end if;
        toneOut <= sa1;
        LED <= (2 => '1', others => '0');

    elsif(switch(3) = '1') then
        if (count_sa1 = 78125) then--320Hz
            count_sa1 := 1;
            sa1 := not sa1;
        else
            count_sa1 := count_sa1 + 1;
        end if;
        toneOut <= sa1;
        LED <= (3 => '1', others => '0');

    elsif(switch(4) = '1') then
        if (count_sa1 = 69444) then--360Hz
            count_sa1 := 1;
            sa1 := not sa1;
        else
            count_sa1 := count_sa1 + 1;
        end if;
        toneOut <= sa1;
        LED <= (4 => '1', others => '0');

    elsif(switch(5) = '1') then
        if (count_sa1 = 62500) then--400Hz

```

```

        count_sa1 := 1;
        sa1 := not sa1;
    else
        count_sa1 := count_sa1 + 1;
    end if;
    toneOut <= sa1;
    LED <= (5 => '1', others => '0');


elsif(switch(6) = '1') then
    if (count_sa1 = 55556) then--450Hz
        count_sa1 := 1;
        sa1 := not sa1;
    else
        count_sa1 := count_sa1 + 1;
    end if;
    toneOut <= sa1;
    LED <= (6 => '1', others => '0');

elsif(switch(7) = '1') then
    if (count_sa1 = 52083) then--480Hz
        count_sa1 := 1;
        sa1 := not sa1;
    else
        count_sa1 := count_sa1 + 1;
    end if;
    toneOut <= sa1;
    LED <= (7 => '1', others => '0');

end if;
end if;
end process;
end behavioral;

```


## RTL View:

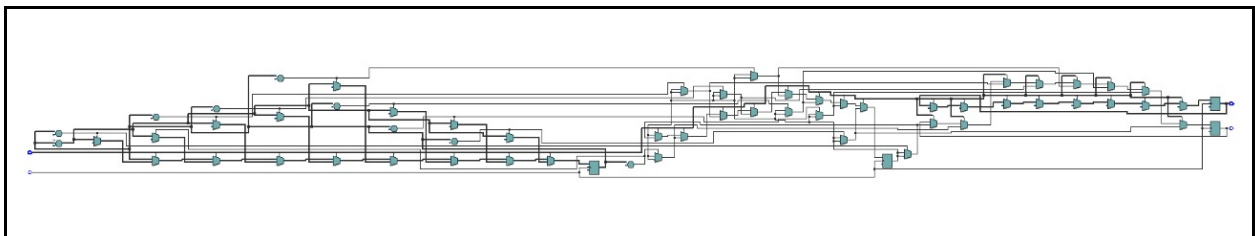

## DUT Input/Output Format:

NA


## RTL Simulation:

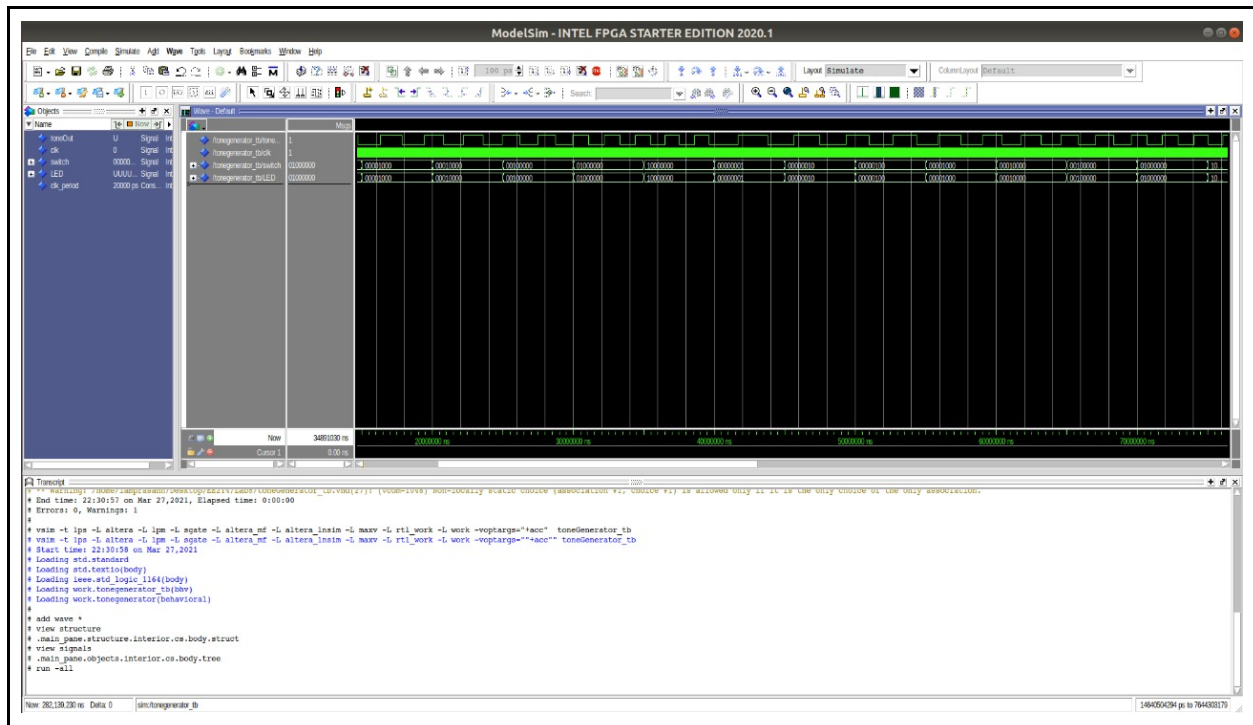


## Gate-level Simulation:

NA

Krypton board\*:

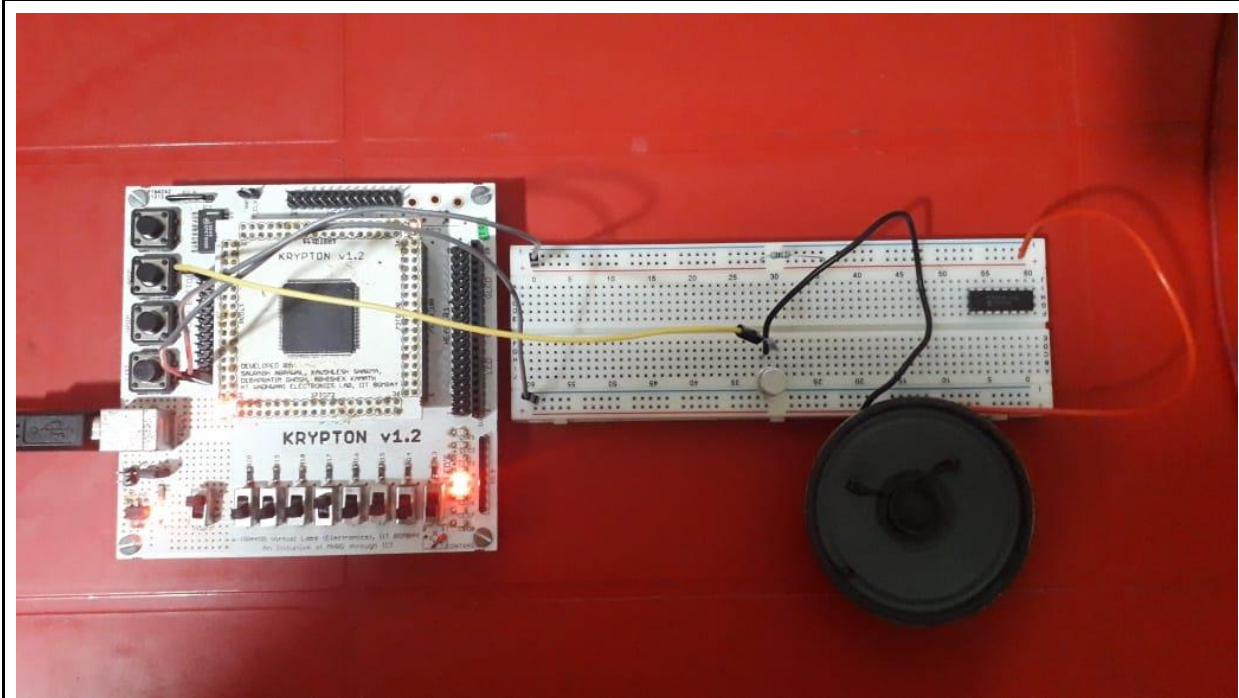


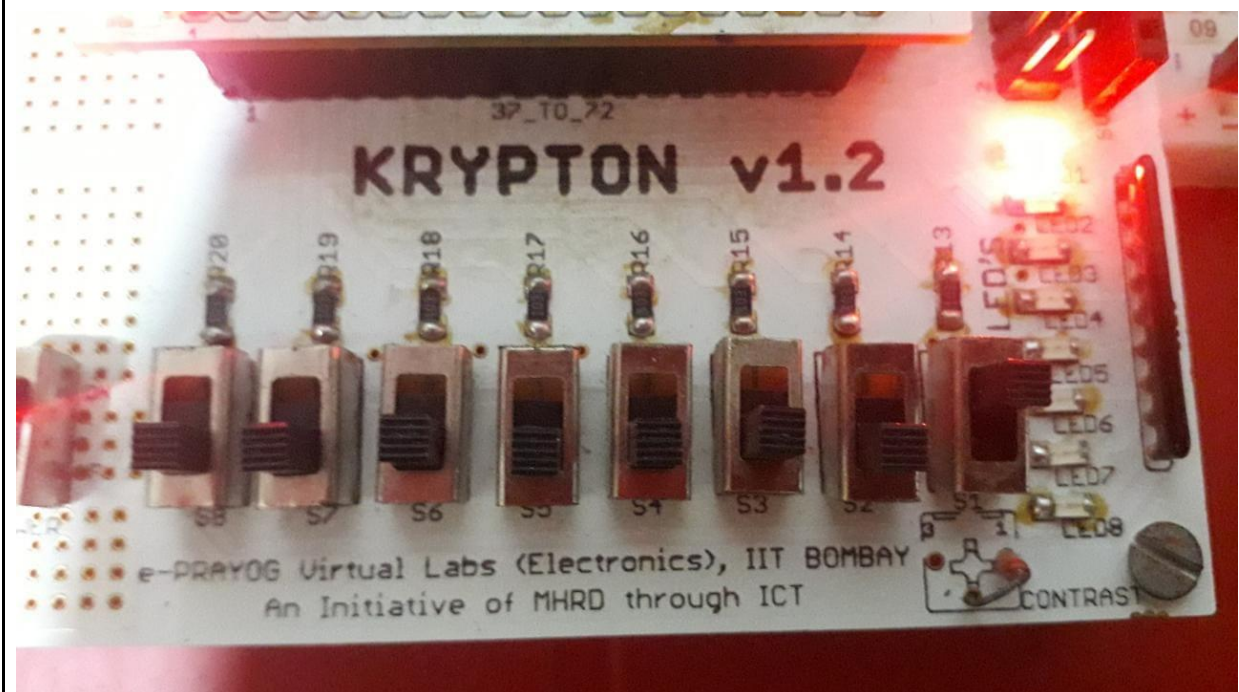Krypton board connected to speaker with proper connections to play music




Switch 1 corresponds to LED1



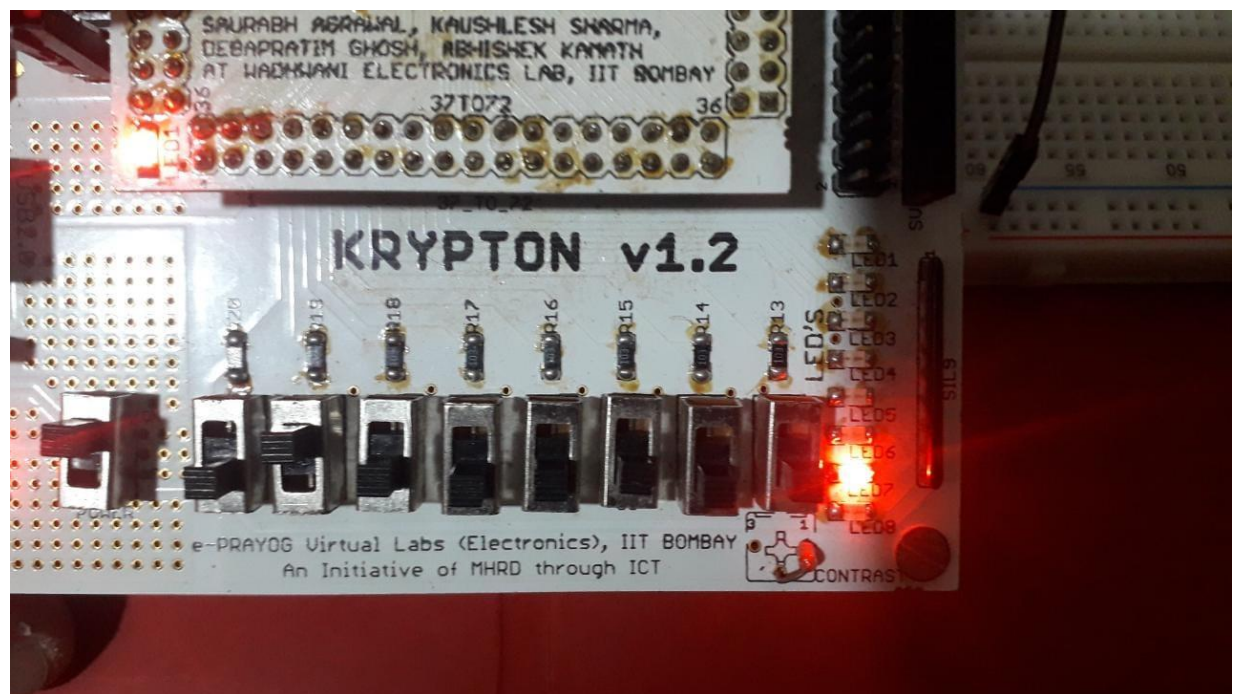

Switch 7 corresponds to LED 7.

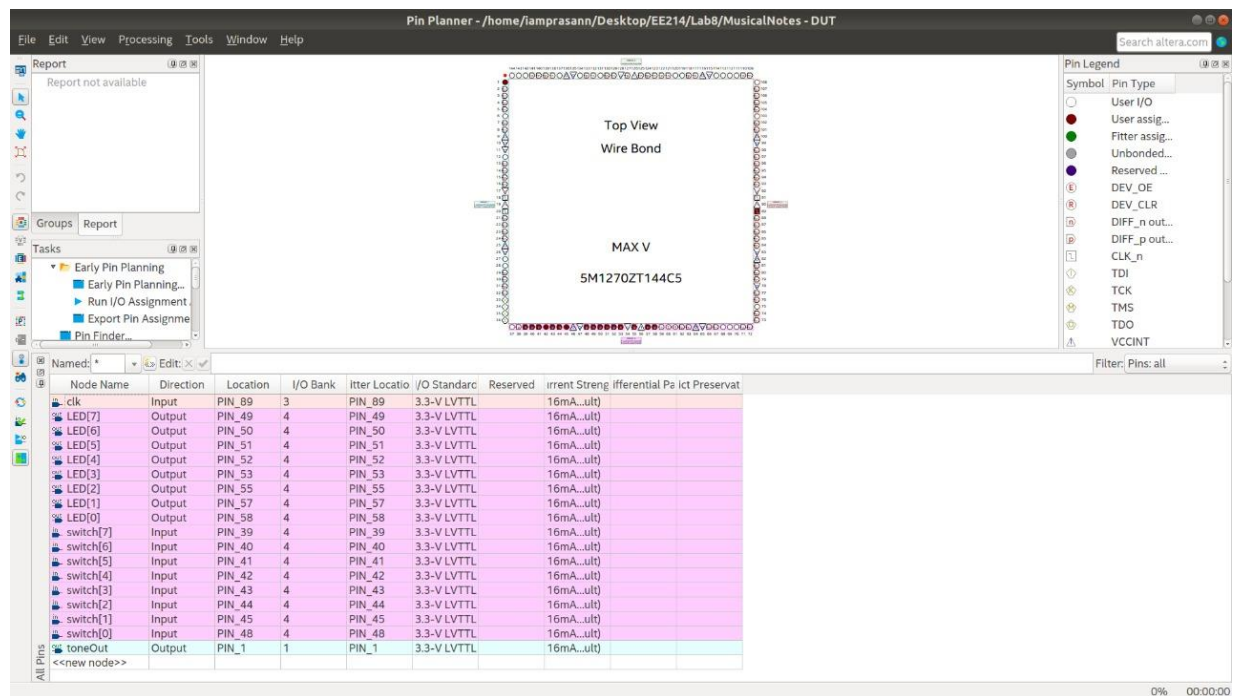

Pin planning shown

## Observations\*:

Sound generated matches that of Indian Ra Ga tones

[https://drive.google.com/file/d/1iKI46898pgyURBS7piD7kgGFXEIol\\_hT/view?usp=sharing](https://drive.google.com/file/d/1iKI46898pgyURBS7piD7kgGFXEIol_hT/view?usp=sharing)

Can view the video of the tones and LEDs at this link. (Better than Moodle Placeholder)

## References:

TA provided codes.