

Experiment 1: Combinational Circuits - I

Prasann Viswanathan, Roll Number 190070047
EE-214, WEL, IIT Bombay
February 20th, 2021

Overview of the experiment:

The purpose of part 1 of the experiment was to design a logical circuit which returns an output of 1 for a prime number input and 0 for a composite number. The number input was four bits, as a result we had to check for decimal values {2, 3, 5, 7, 11, 13} only. I implemented this circuit using AND, OR, NOT gates only.


The purpose of part 2 of the experiment was to use the algorithm developed in part 1 in order to create a logical unit which performs different instructions based on whether the input binary numbers A and B were prime or composite. I implemented this circuit using the check prime logical unit from part 1, as well as four-bit adder we had created earlier and 4 input multiplexer.

For part 1 I started with the Kmap minimization for 4 bit inputs a_3, \dots, a_0 . This gave a fairly easy circuit to implement with 4 product terms of size 3 each. With this in mind, I had to build a 3 input AND and a 4 input OR gate for easy implementation of the Kmap minimization. Then I finished the part 1 DUT file and made few changes to the Testbench. I generated a TRACEFILE.txt using python. Finally I ran all simulations - RTL and Gate Level to check if everything was proper. Then I implemented this on the Krypton board provided using URJtag software. On confirmation with the TA everything was proper.


For part 2 I abstracted the check prime entity as a basic logical unit returning 1 and 0 based on whether the input was prime or not. As a result this prime/not prime value became my select input for my multiplexers. The remaining was implemented via four bit adder created in a previous lab. I stored the addition and subtraction value of A and B and these different values became the 4 inputs for each of the 5 MUXes. Then I finished the DUT and Testbench and used the TRACEFILE provided to us by our TA. I checked the simulations - RTL and Gate Level and everything worked. I implemented this on Krypton board. Finally, in the subsequent lab we used scan chain along with TIVA C to implement a more efficient testing system for the krypton board and demonstrated that as well to our TA.

Approach to the experiment:

Part 1:

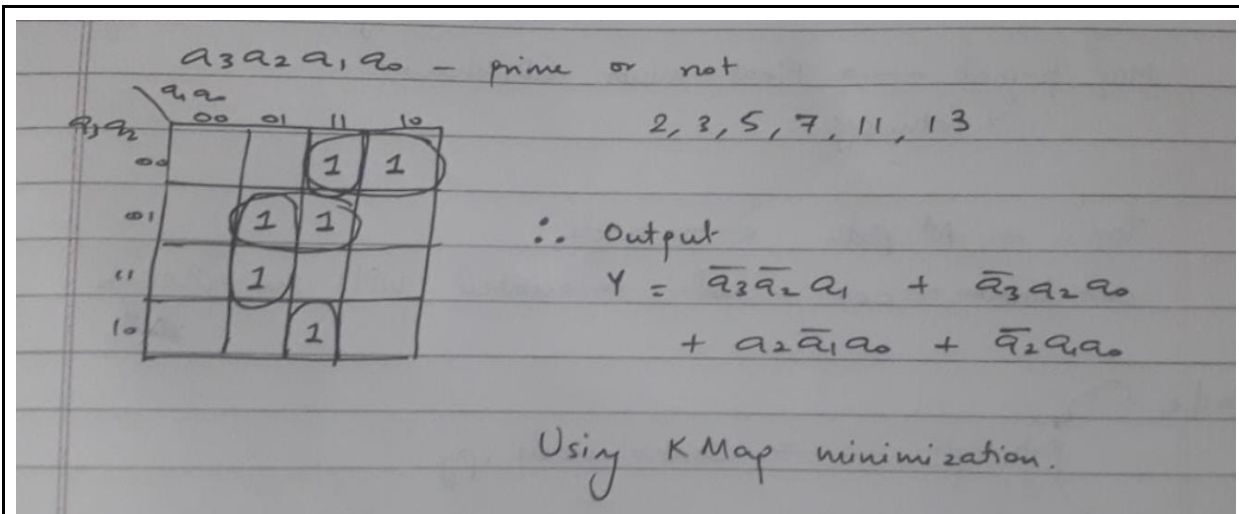

Part 2:

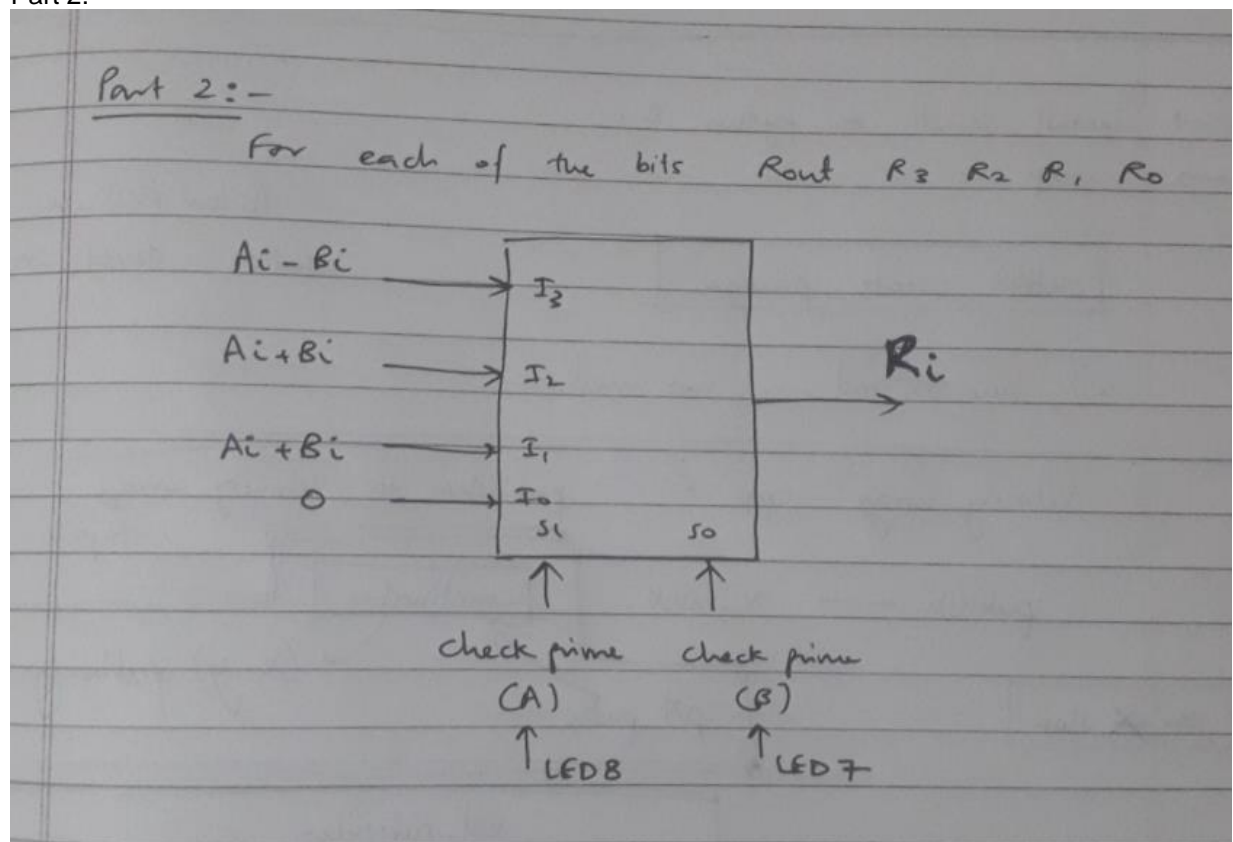

The logic behind generating these was previously explained in Overview.

Design document and VHDL code if relevant:

DUT: Wraps the Check_Prime entity and converts the inputs and outputs to be std logic vectors.

Testbench: Compares outputs of TRACEFILE.txt and output of implementation.

AND_3: 3 input and component made from 2 input ANDS

OR_4: 4 input or component made from 2 input ORS

Check_Prime: Main logic which implements the KMAP minimized formula in order to check if the number input is prime or not.

Architecture of Check_Prime:

architecture Struct of Check_Prime is

```
    component AND_3 is
        port (A, B, C: in std_logic; Y: out std_logic);
    end component AND_3;
```

```
    component INVERTER is
        port (A: in std_logic; Y: out std_logic);
    end component INVERTER;
```

```
    component OR_4 is
        port (A, B, C, D: in std_logic; Y: out std_logic);
    end component OR_4;
```

```
-- Signal names are self sufficient to understand when paired with component port maps
signal I1, I2, I3, O1, O2, O3, O4: std_logic;
```

begin

```
-- component instances
```

```
not1: INVERTER
    port map(A=>A1, Y=>I1);
```

```
not2: INVERTER
    port map(A=>A2, Y=>I2);
```

```
not3: INVERTER
    port map(A=>A3, Y=>I3);
```

```
and1: AND_3
    port map(A=>I2, B=>A1, C=>A0, Y=>O1);
```

```
and2: AND_3
    port map(A=>I3, B=>I2, C=>A1, Y=>O2);
```

```
and3: AND_3
    port map(A=>I3, B=>A2, C=>A0, Y=>O3);
```

```
and4: AND_3
    port map(A=>A2, B=>I1, C=>A0, Y=>O4);
```

```
or_final: OR_4
    port map(A=>O1, B=>O2, C=>O3, D=>O4, Y=>Y);
```

end Struct;

End of Part 1

DUT: Wraps the Add_Subtract_Prime entity and converts the inputs and outputs to be std logic vectors.

Testbench: Compares outputs of TRACEFILE.txt and output of implementation.

Check_Prime: Previously implemented reused code.

Four_Bit_Adder: Previously implemented Four Bit Adder code.

Four_MUX: Previously implemented Four Input MUX

TwosComp: Algorithm to convert a 4 bit number to it's 2's complement.

Add_Subtract_Primes: Main logic to implement addition subtraction of numbers based on the select input for MUX.

Architecture of Add_Subtract_Primes:

architecture Struct of Add_Subtract_Primes is

```
    component Check_Prime is
        port (A3, A2, A1, A0: in std_logic; Y: out std_logic);
    end component Check_Prime;
```

```
    component Four_Bit_Adder is
        port (A0, A1, A2, A3, B0, B1, B2, B3: in std_logic; R0, R1, R2, R3, Cout: out std_logic);
    end component Four_Bit_Adder;
```

```
    component TwosComp is
        port (X1, X2, X3, X4: in std_logic; Y1, Y2, Y3, Y4: out std_logic);
    end component TwosComp;
```

```
    component FourIPMUX is
        port (X1, X2, X3, X4, S1, S2: in std_logic; Y: out std_logic);
    end component FourIPMUX;
```

```
    component INVERTER is
        port (A: in std_logic; Y: out std_logic);
    end component INVERTER;
```

```
    -- Signal names are self sufficient to understand when paired with component port maps
    signal Log1, Log2, I0, I1, I2, I3, Sub0, Sub1, Sub2, Sub3, CSFinal, CarrySub, Add0, Add1,
    Add2, Add3, CarryAdd: std_logic;
```

begin

```
    -- component instances
    logical1: Check_Prime
        port map(A3=>A3, A2=>A2, A1=>A1, A0=>A0, Y=>Log1);
```

```
    logical2: Check_Prime
        port map(A3=>B3, A2=>B2, A1=>B1, A0=>B0, Y=>Log2);
```

```
    minus_b: TwosComp
        port map(B0, B1, B2, B3, I0, I1, I2, I3);
```

```
    sub: Four_Bit_Adder
        port map(A0, A1, A2, A3, I0, I1, I2, I3, Sub0, Sub1, Sub2, Sub3, CarrySub);
```

```
    add: Four_Bit_Adder
        port map(A0, A1, A2, A3, B0, B1, B2, B3, Add0, Add1, Add2, Add3, CarryAdd);
```

```
    mux1: FourIPMUX
```

```

port map('0', Add0, Add0, Sub0, Log1, Log2, R0);

mux2: FourIPMUX
port map('0', Add1, Add1, Sub1, Log1, Log2, R1);

mux3: FourIPMUX
port map('0', Add2, Add2, Sub2, Log1, Log2, R2);

mux4: FourIPMUX
port map('0', Add3, Add3, Sub3, Log1, Log2, R3);

inv : INVERTER
port map(CarrySub, CSFinal);

mux5: FourIPMUX
port map('0', CarryAdd, CarryAdd, CSFinal, Log1, Log2, Cout);


L1 <= Log1;
L2 <= Log2;
end Struct;

```


End of Part 2

RTL View:

Part 1:

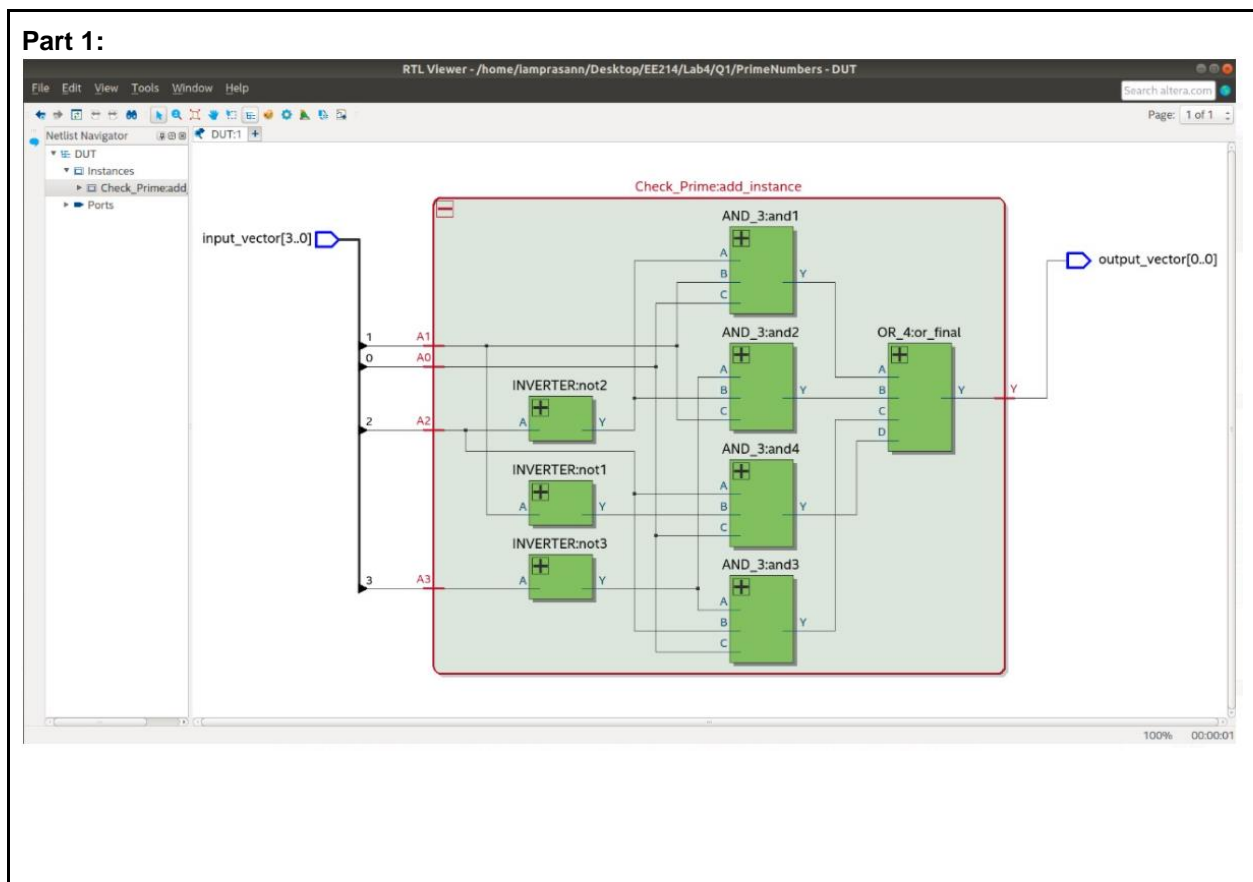

Part 2:

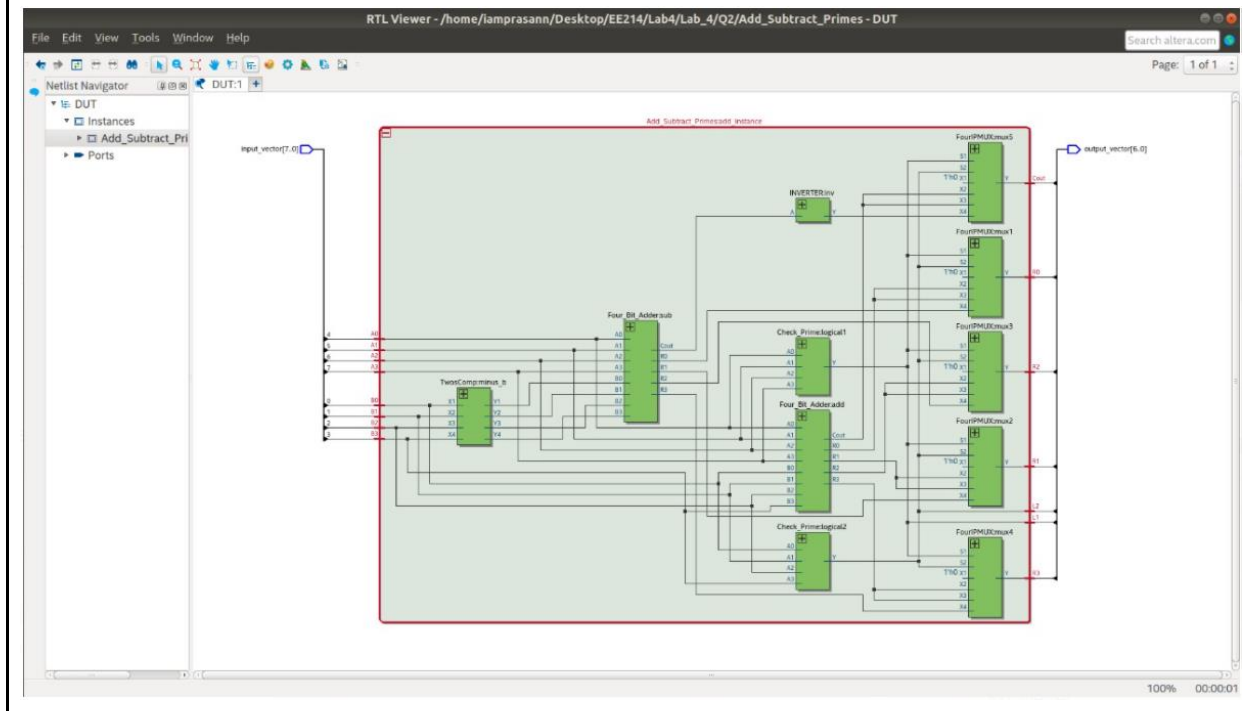

DUT Input/Output Format:

Part 1:

Input is a std logic vector of size 4. The LSB of the input is a0 and the MSB of the input is a3.
Output is a std logic vector of size 1. It is just the truth value of whether the 4 bit number is prime.

```
0110 0 1
0111 1 1
1000 0 1
1001 0 1
1010 0 1
1011 1 1
1100 0 1
```

(Note 7 and 11 are Prime)

Part 2:

Input is a std logic vector of size 8. The lower nibble is B3-B0 and upper nibble A3-A0.
Output is a std logic vector of size 7. The MSBs are truth value of primes and lower 5 bits are the arithmetic output.

```
00001010 0000000 1111111
00001011 0101011 1111111
00001100 0000000 1111111
00001101 0101101 1111111
00001110 0000000 1111111
```

```


00001111 0000000 1111111
00010000 0000000 1111111
00010001 0000000 1111111
00010010 0100011 1111111
00010011 0100100 1111111
00010100 0000000 1111111

```


Examples of some cases: Can check that if either is prime we are adding and if both are prime we subtract. Finally if both composite, our output is 0.

RTL Simulation:

Part 1:

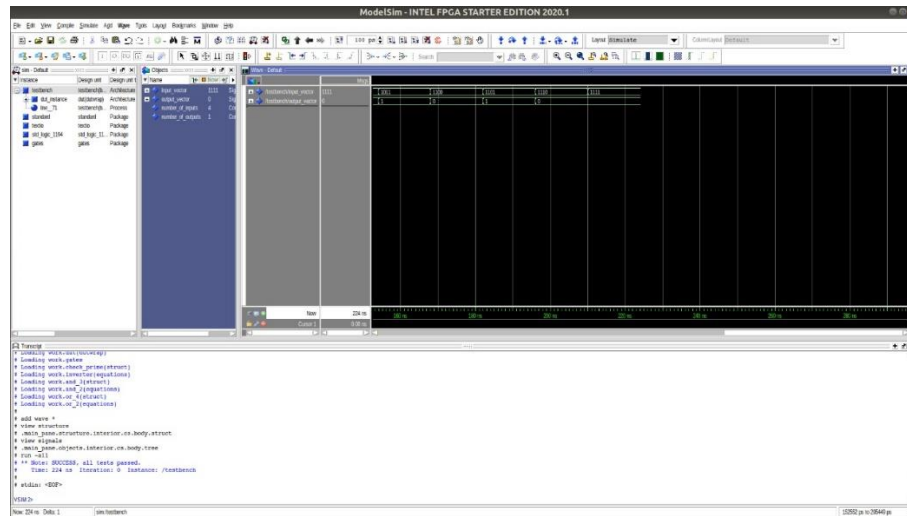

Part 2:

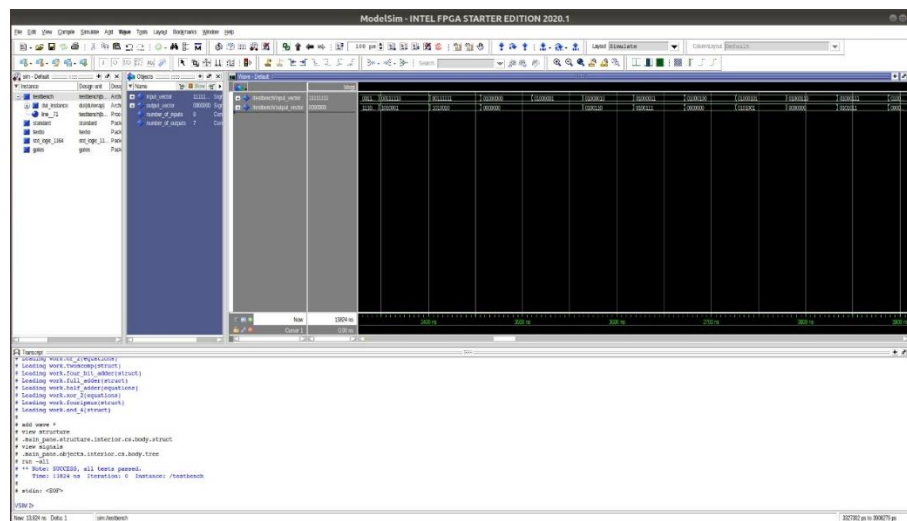

Part 1:

The screenshot shows the ModelSim interface with the testbench file `testbench.vhd` loaded. The simulation has completed successfully at 224 ns. The console output shows the following messages:

```

VSM>
New 224 ns Delta 1
simtestbench
0 ps to 23920 ps

```

Part 2:

The screenshot shows the ModelSim interface with the testbench file `testbench.vhd` loaded. The simulation has completed successfully at 13824 ns. The console output shows the following messages:

```

VSM>
New 13824 ns Delta 1
simtestbench
0 ps to 54020 ps

```


Pin Planning Part 1:

Pin Planner - /home/lamprasann/Desktop/EE214/Lab4/Q1/PrimeNumbers - DUT

Report not available

Groups Report

Tasks

- Early Pin Planning
 - Early Pin Planning...
 - Run I/O Assignment
 - Export Pin Assignment
- Pin Finder...
- Highlight Pins
- I/O Banks
- Edges

Named: * Edit: X

Node Name	Direction	Location	I/O Bank	I/O Standard	Reserved	Current Strength	Differential	Pair	Preserve
input_vector[3]	Input	PIN_43	4	3.3-V...alt		16mA...alt			
input_vector[2]	Input	PIN_44	4	3.3-V...alt		16mA...alt			
input_vector[1]	Input	PIN_45	4	3.3-V...alt		16mA...alt			
input_vector[0]	Input	PIN_48	4	3.3-V...alt		16mA...alt			
output_vector[0]	Output	PIN_49	4	3.3-V...alt		16mA...alt			
<<new node>>									

Filter: Pins: all

0% 00:00:00

Pin Planning Part 2:

Pin Planner - /home/lamprasann/Desktop/EE214/Lab4/Lab_4/Q2/Add_Subtract_Primes - DUT

Report not available

Groups Report

Tasks

- Early Pin Planning
 - Early Pin Planning...
 - Run I/O Assignment
 - Export Pin Assignment
- Pin Finder...
- Highlight Pins
- I/O Banks
- Edges

Named: * Edit: X

Node Name	Direction	Location	I/O Bank	I/O Standard	Reserved	Current Strength	Differential	Pair	Preserve
input_vector[7]	Input	PIN_39	4	3.3-V...alt		16mA...alt			
input_vector[6]	Input	PIN_40	4	3.3-V...alt		16mA...alt			
input_vector[5]	Input	PIN_41	4	3.3-V...alt		16mA...alt			
input_vector[4]	Input	PIN_42	4	3.3-V...alt		16mA...alt			
input_vector[3]	Input	PIN_43	4	3.3-V...alt		16mA...alt			
input_vector[2]	Input	PIN_44	4	3.3-V...alt		16mA...alt			
input_vector[1]	Input	PIN_45	4	3.3-V...alt		16mA...alt			
input_vector[0]	Input	PIN_48	4	3.3-V...alt		16mA...alt			
output_vector[6]	Output	PIN_49	4	3.3-V...alt		16mA...alt			
output_vector[5]	Output	PIN_50	4	3.3-V...alt		16mA...alt			
output_vector[4]	Output	PIN_52	4	3.3-V...alt		16mA...alt			
output_vector[3]	Output	PIN_53	4	3.3-V...alt		16mA...alt			
output_vector[2]	Output	PIN_55	4	3.3-V...alt		16mA...alt			
output_vector[1]	Output	PIN_57	4	3.3-V...alt		16mA...alt			
output_vector[0]	Output	PIN_58	4	3.3-V...alt		16mA...alt			
<<new node>>									

Filter: Pins: all

0% 00:00:00

Pin Planning Part 2:

	Node Name	Direction	Location	I/O Bank	I/O Standard	Reserved	Current Strength	Differential Pair	IO Protection
	input_vector[3]	Input	PIN_43	4	3.3-V _{ALT}		16mA _{AULT}		
	input_vector[2]	Input	PIN_44	4	3.3-V _{ALT}		16mA _{AULT}		
	input_vector[1]	Input	PIN_45	4	3.3-V _{ALT}		16mA _{AULT}		
	input_vector[0]	Input	PIN_48	4	3.3-V _{ALT}		16mA _{AULT}		
	output_vector[0]	Output	PIN_49	4	3.3-V _{ALT}		16mA _{AULT}		
	<new node>								

	Node Name	Direction	Location	I/O Bank	/O Standard	Reserved	Imm Stren	fferential Pa	ct Preserv
PINS	input_vector[7]	Input	PIN_39	4	3.3-V _{AUT}		16mA _{AUT}		
	input_vector[6]	Input	PIN_40	4	3.3-V _{AUT}		16mA _{AUT}		
	input_vector[5]	Input	PIN_41	4	3.3-V _{AUT}		16mA _{AUT}		
	input_vector[4]	Input	PIN_42	4	3.3-V _{AUT}		16mA _{AUT}		
	input_vector[3]	Input	PIN_43	4	3.3-V _{AUT}		16mA _{AUT}		
	input_vector[2]	Input	PIN_44	4	3.3-V _{AUT}		16mA _{AUT}		
	input_vector[1]	Input	PIN_45	4	3.3-V _{AUT}		16mA _{AUT}		
	input_vector[0]	Input	PIN_48	4	3.3-V _{AUT}		16mA _{AUT}		
	output_...ctor[6]	Output	PIN_49	4	3.3-V _{AUT}		16mA _{AUT}		
	output_...ctor[5]	Output	PIN_50	4	3.3-V _{AUT}		16mA _{AUT}		
	output_...ctor[4]	Output	PIN_52	4	3.3-V _{AUT}		16mA _{AUT}		
	output_...ctor[3]	Output	PIN_53	4	3.3-V _{AUT}		16mA _{AUT}		
	output_...ctor[2]	Output	PIN_55	4	3.3-V _{AUT}		16mA _{AUT}		
	output_...ctor[1]	Output	PIN_57	4	3.3-V _{AUT}		16mA _{AUT}		
	output_...ctor[0]	Output	PIN_58	4	3.3-V _{AUT}		16mA _{AUT}		

Switches Part 1:



Fig 1 – IP (1101 – 13 decimal) OP Prime (LED ON)

Fig 2 – IP (0100 – 4 decimal) OP Composite (LED OFF)

Switches Part 2:



Fig 1 – IP (A=13, B=7) OP(R=6) Both LEDS 7,8 on as 13 and 7 Prime


Fig 2 – IP (A=5, B=4) OP(R=9) LEDS 8 on as only 5 Prime




Fig 3 – IP (A=4, B=7) OP(R=11) LEDS 7 on as only 7 Prime

Fig 4 – IP (A=4, B=4) OP(R=0) All LEDS off as A and B = 4 are both composite


Scan Chain Part 2:

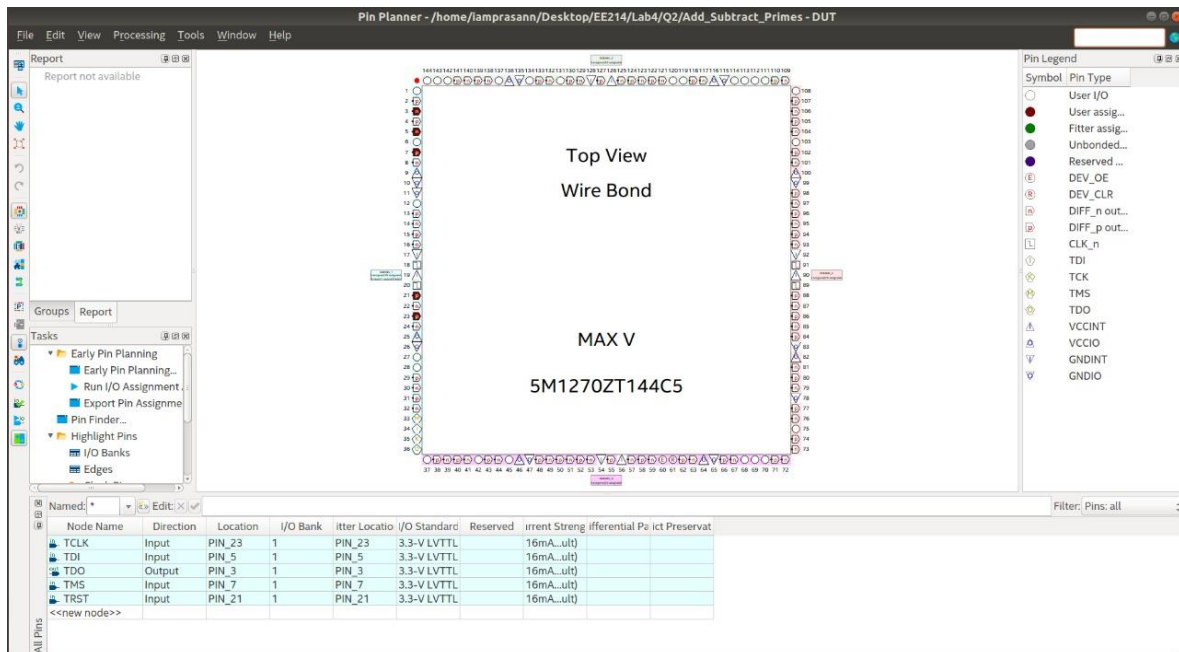

Connections on Krypton and Tiva:

 

Outputs Passed:

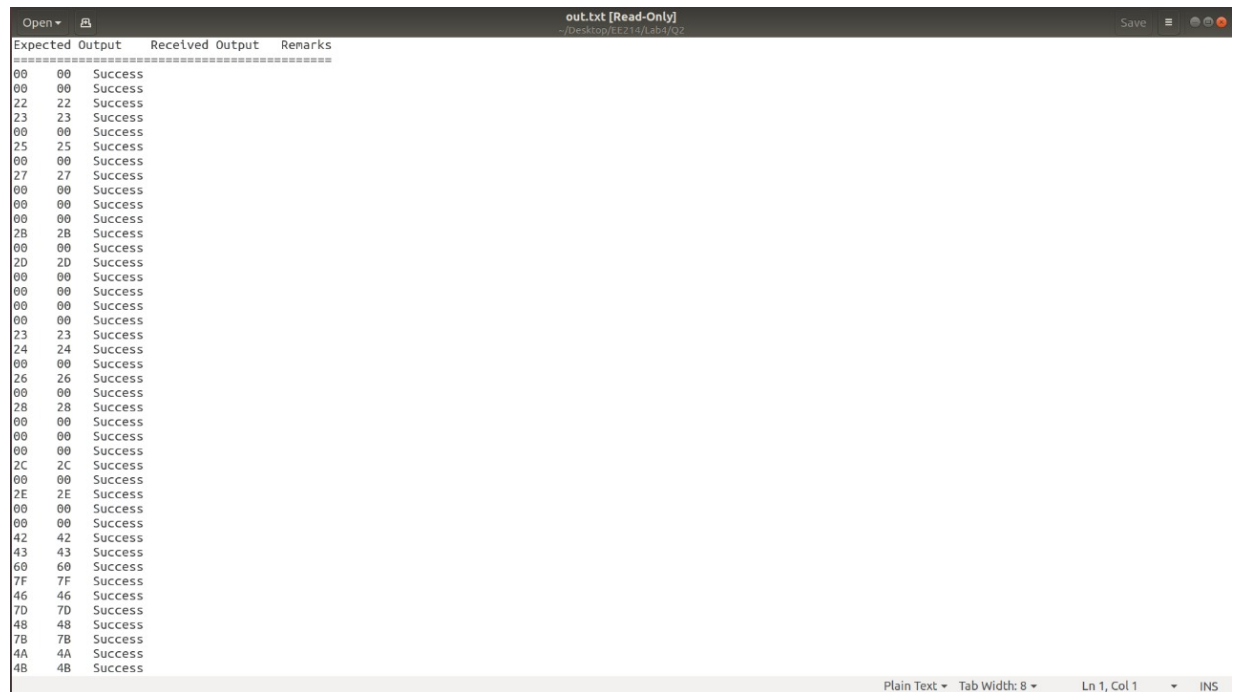

Expected Output	Received Output	Remarks
00	00	Success
00	00	Success
22	22	Success
23	23	Success
00	00	Success
25	25	Success
00	00	Success
27	27	Success
00	00	Success
00	00	Success
00	00	Success
2B	2B	Success
00	00	Success
2D	2D	Success
00	00	Success
00	00	Success
00	00	Success
00	00	Success
23	23	Success
24	24	Success
00	00	Success
26	26	Success
00	00	Success
28	28	Success
00	00	Success
00	00	Success
00	00	Success
00	00	Success
2C	2C	Success
00	00	Success
2E	2E	Success
00	00	Success
00	00	Success
42	42	Success
43	43	Success
60	60	Success
7F	7F	Success
46	46	Success
7D	7D	Success
48	48	Success
7B	7B	Success
4A	4A	Success
4B	4B	Success

Observations:

Part 1: The switches S1-S4 acted as input bits with S4 as MSB and S1 as LSB. If the input number was a prime number, LED 8 turns on otherwise it is off. Images attached in Krypton board part.

Part 2: Switch 5-8 acted as input bits for A. The switches 1-4 acted as input bits for B. LED 8 is turned on if A is a prime number and LED 7 is turned on if B is a prime number. The LEDs 1-5 show the output of the operation performed on A and B, represented as R and Rcarry.

Case 1: Both numbers are prime. Both LEDs 8 & 7 are turned on. LEDs 5-1 denotes the result of subtracting 'b' from 'a'. LED 5 denotes the carry bit. LED 4 is the MSB while LED 1 is the LSB of the subtraction result.

Case 2: If either of the numbers is prime. Corresponding LED 8 or 7 is turned on. LEDs 5-1 denote the addition result of 'a' and 'b'. LED 5 denotes the carry bit. LED 4 is the MSB while LED 1 is the LSB of the addition result.

Case 3: If both the numbers are not prime then all LEDs remain off.

References:

NA

